

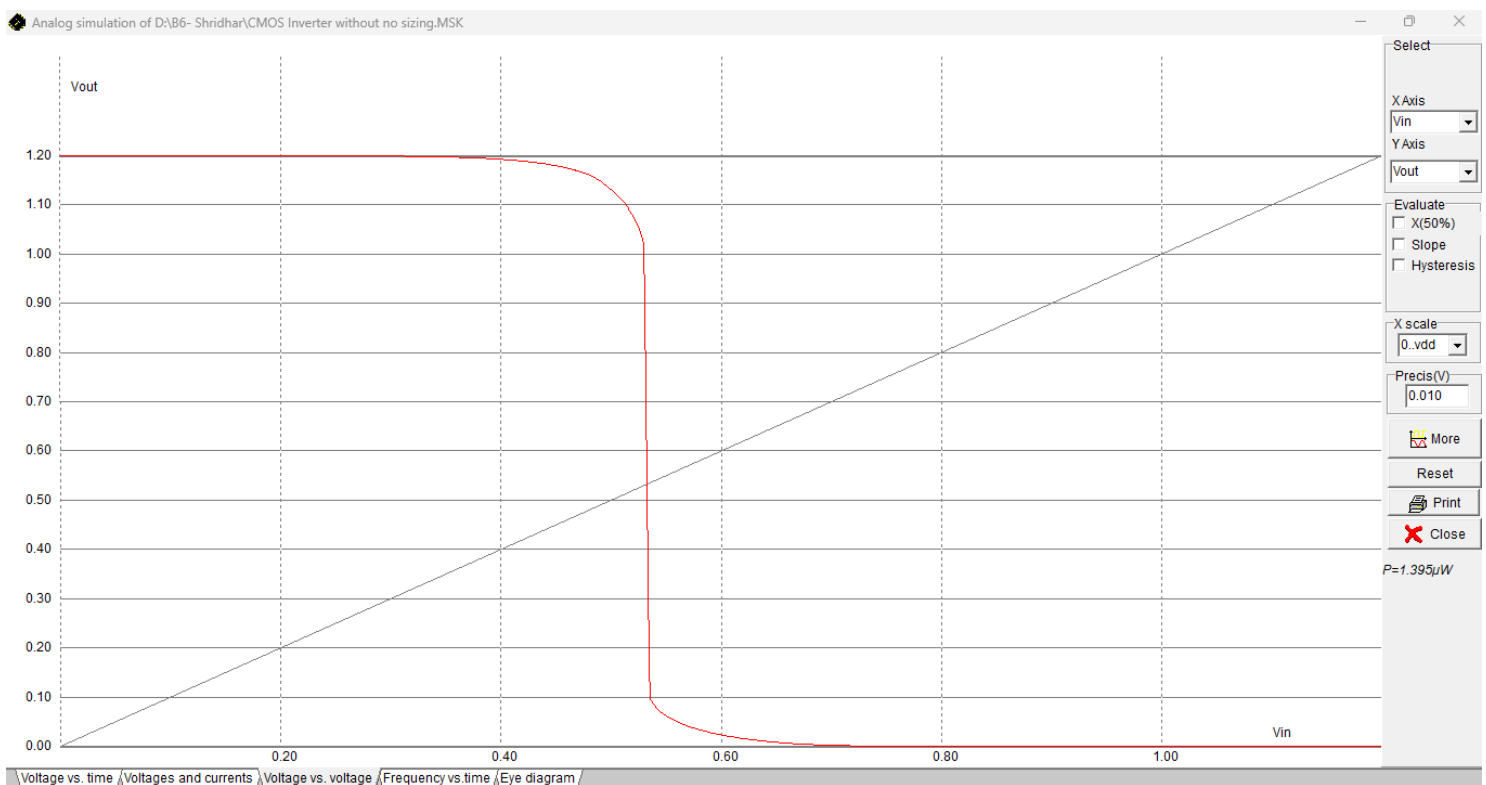
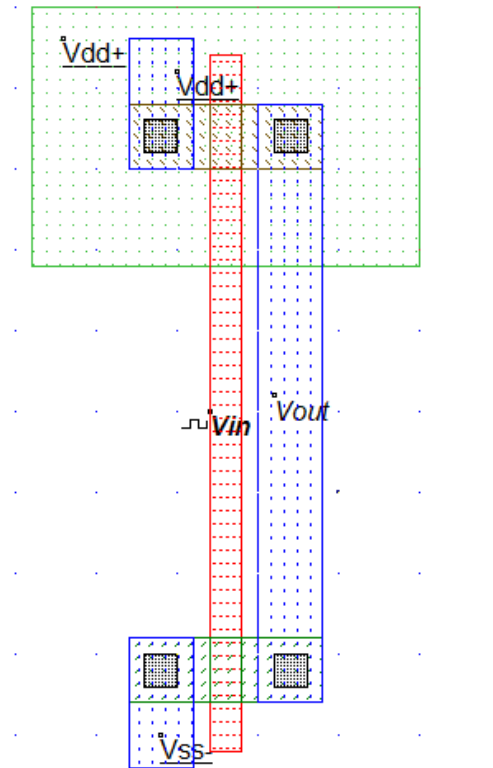
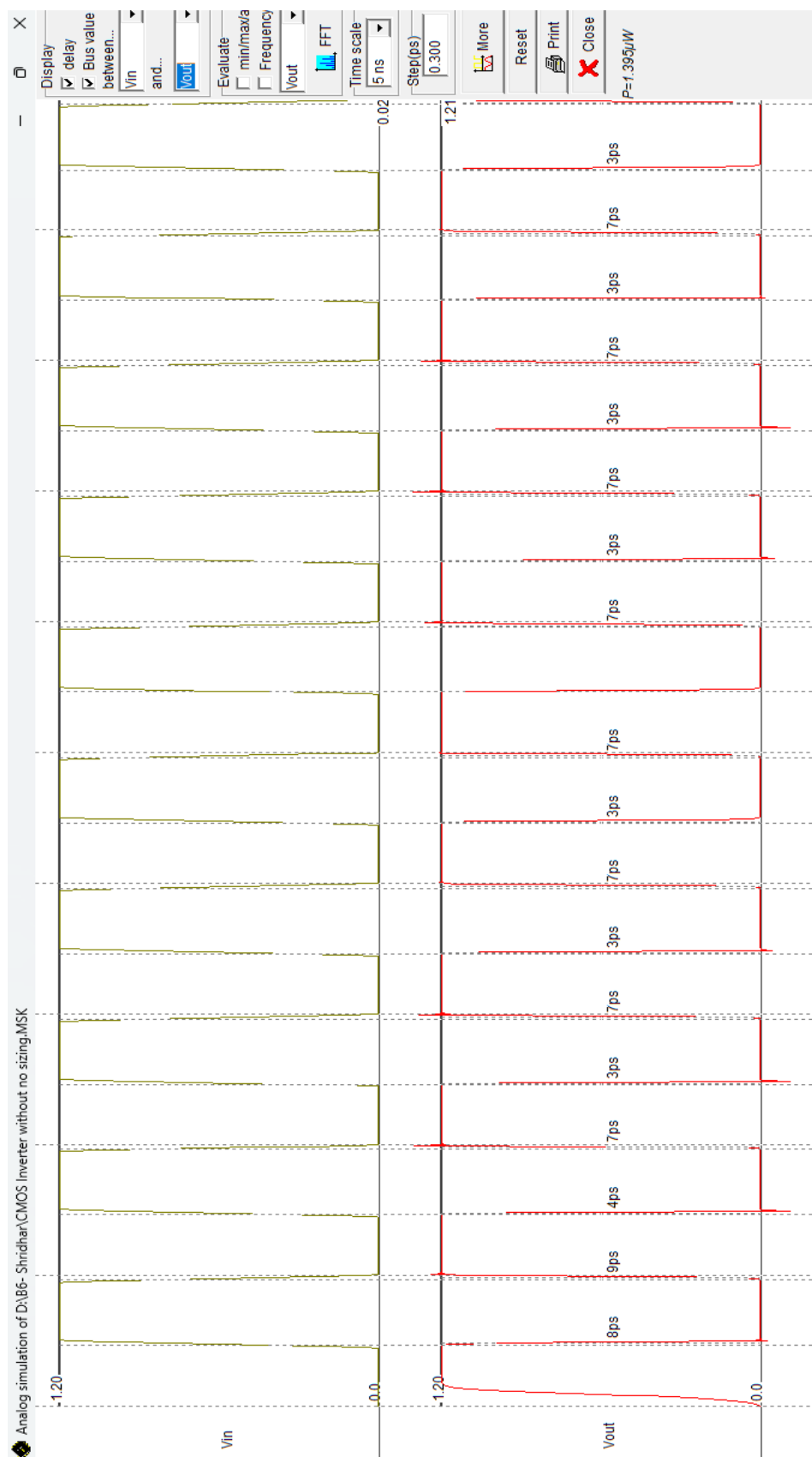
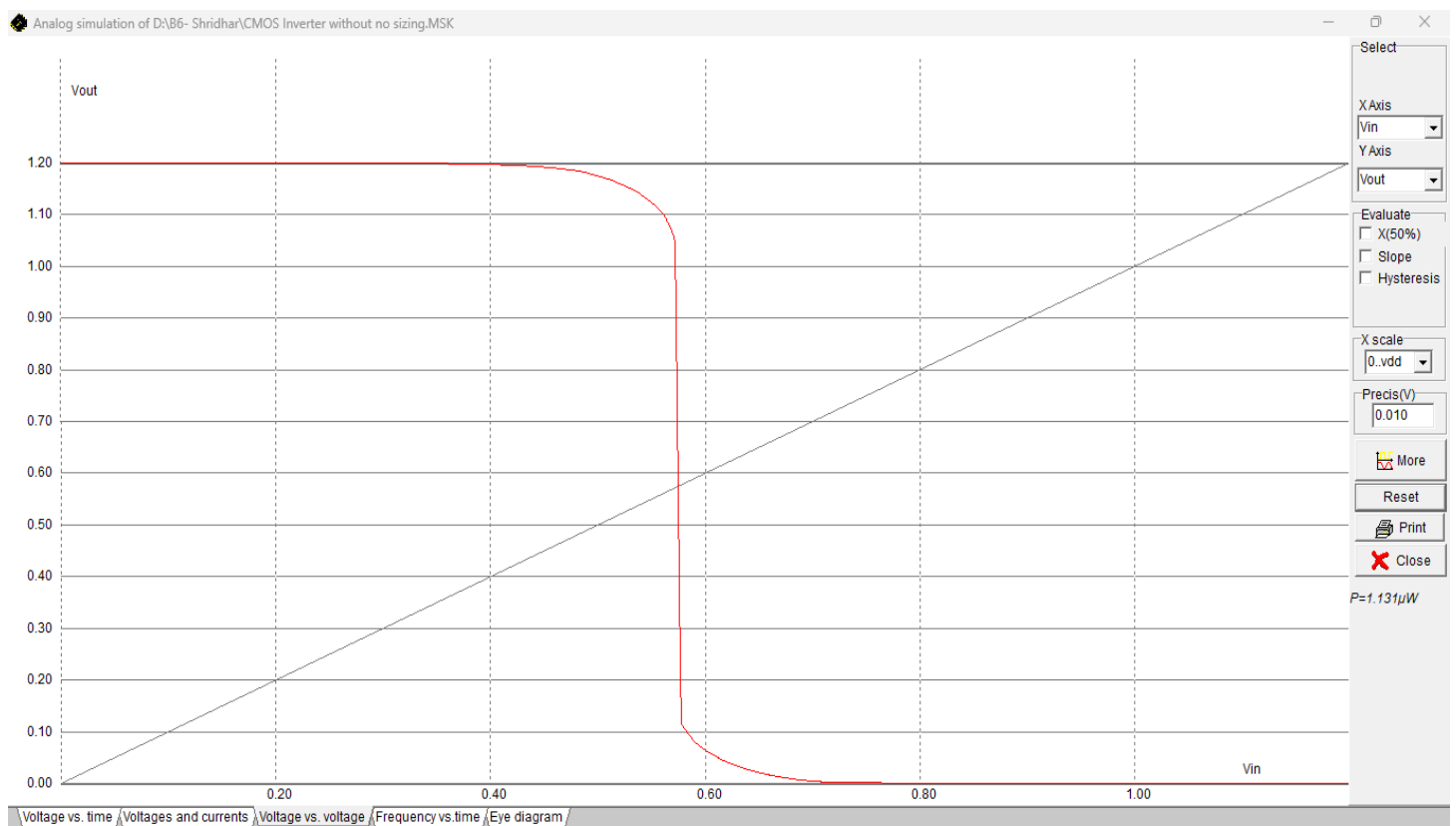



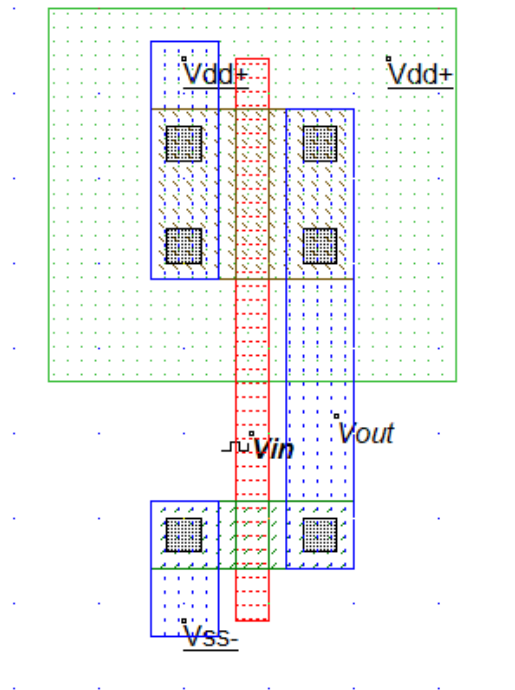
CMOS INVERTER WITHOUT SIZING AND WITHOUT LOAD CAPACITANCE





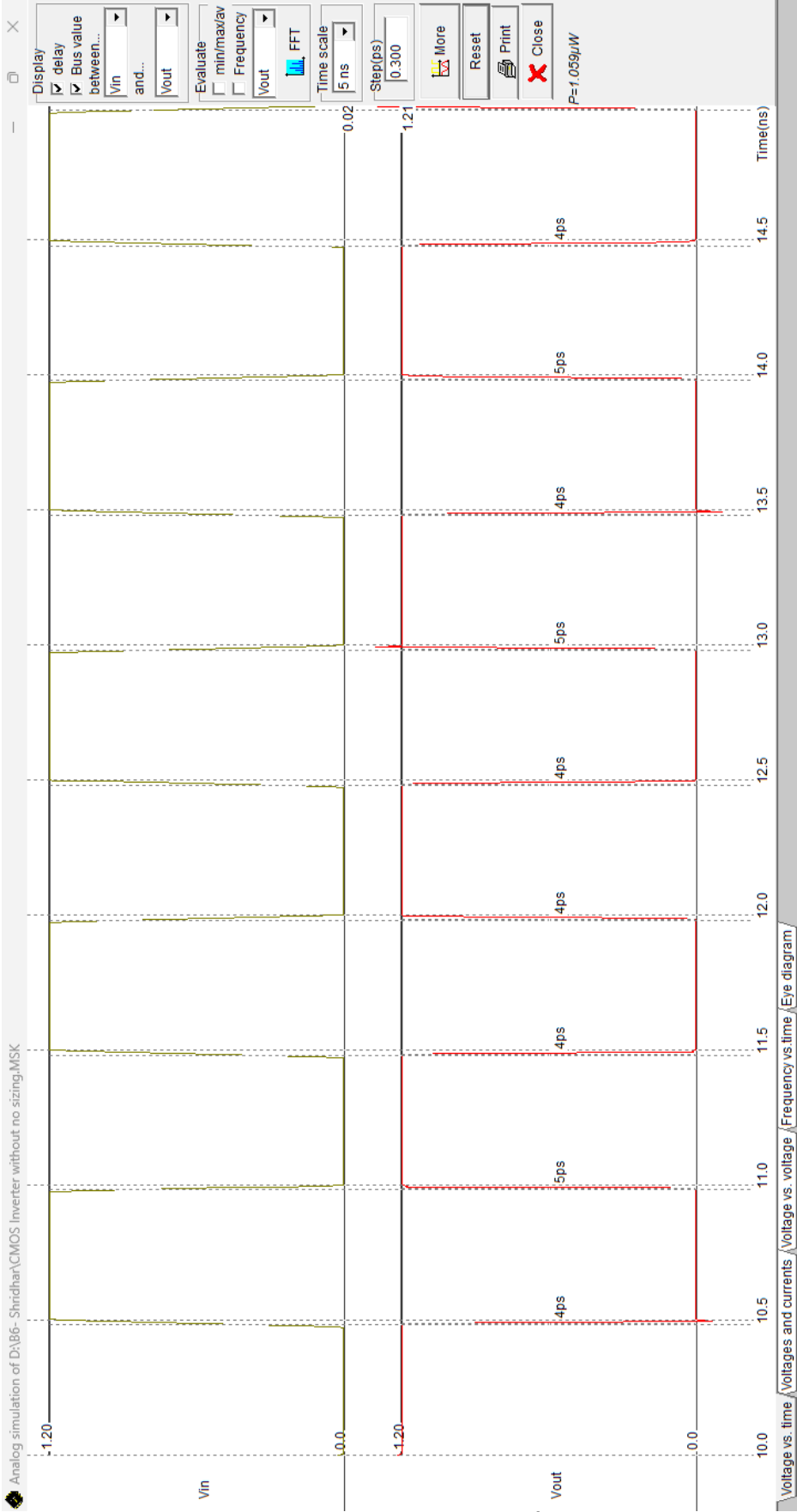
CMOS INVERTER WITH SIZING AND WITHOUT LOAD CAPACITANCE




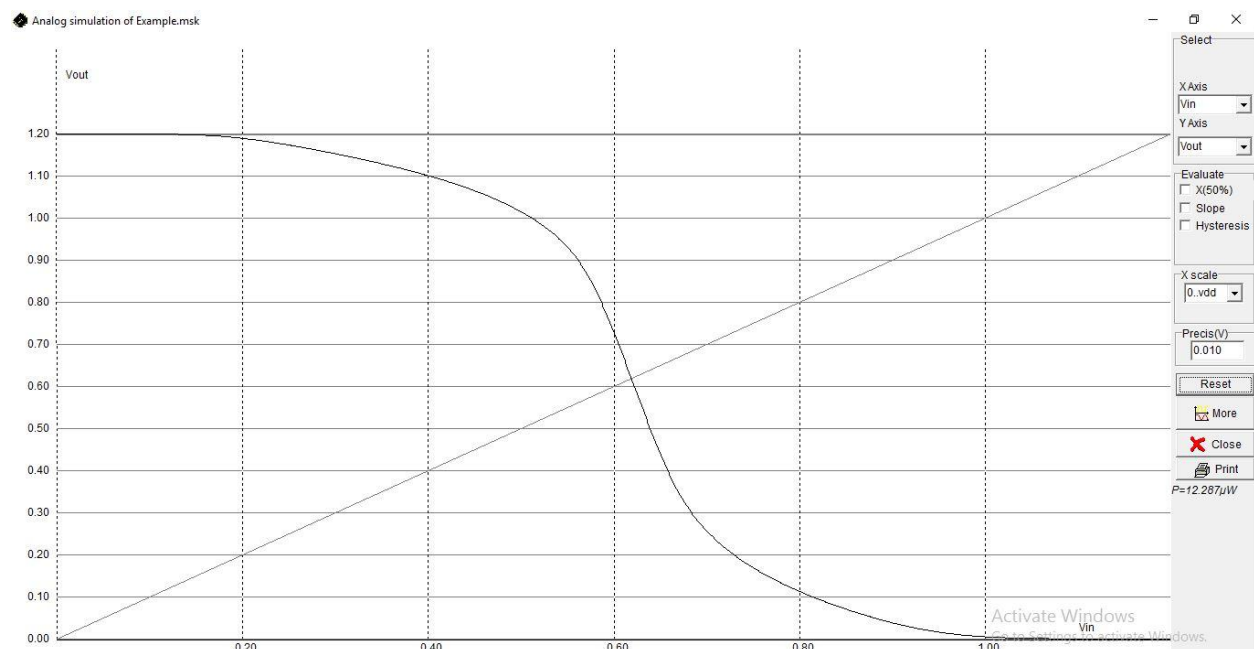
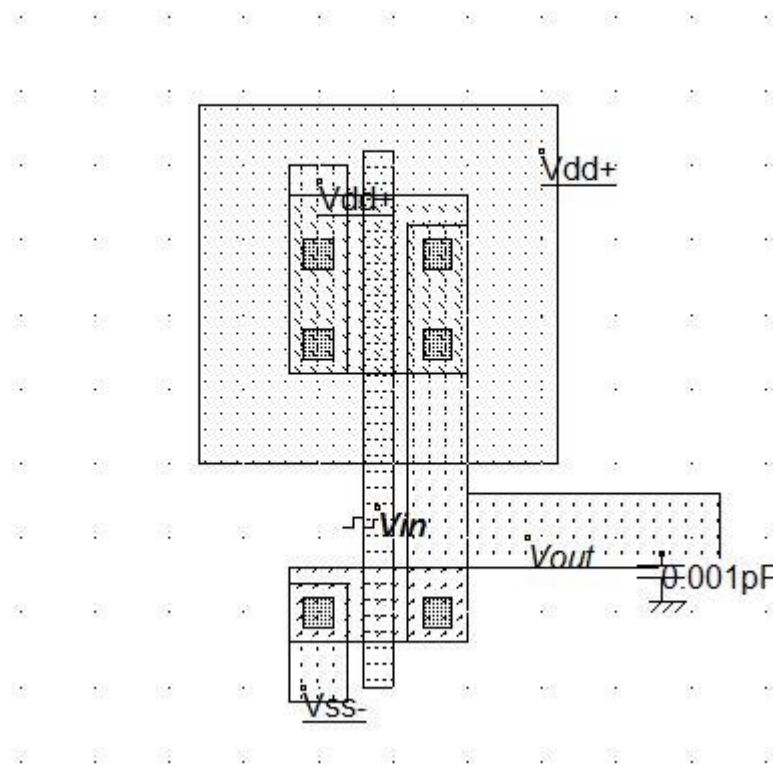
CMOS INVERTER WITH SIZING AND LOAD CAPACITANCE





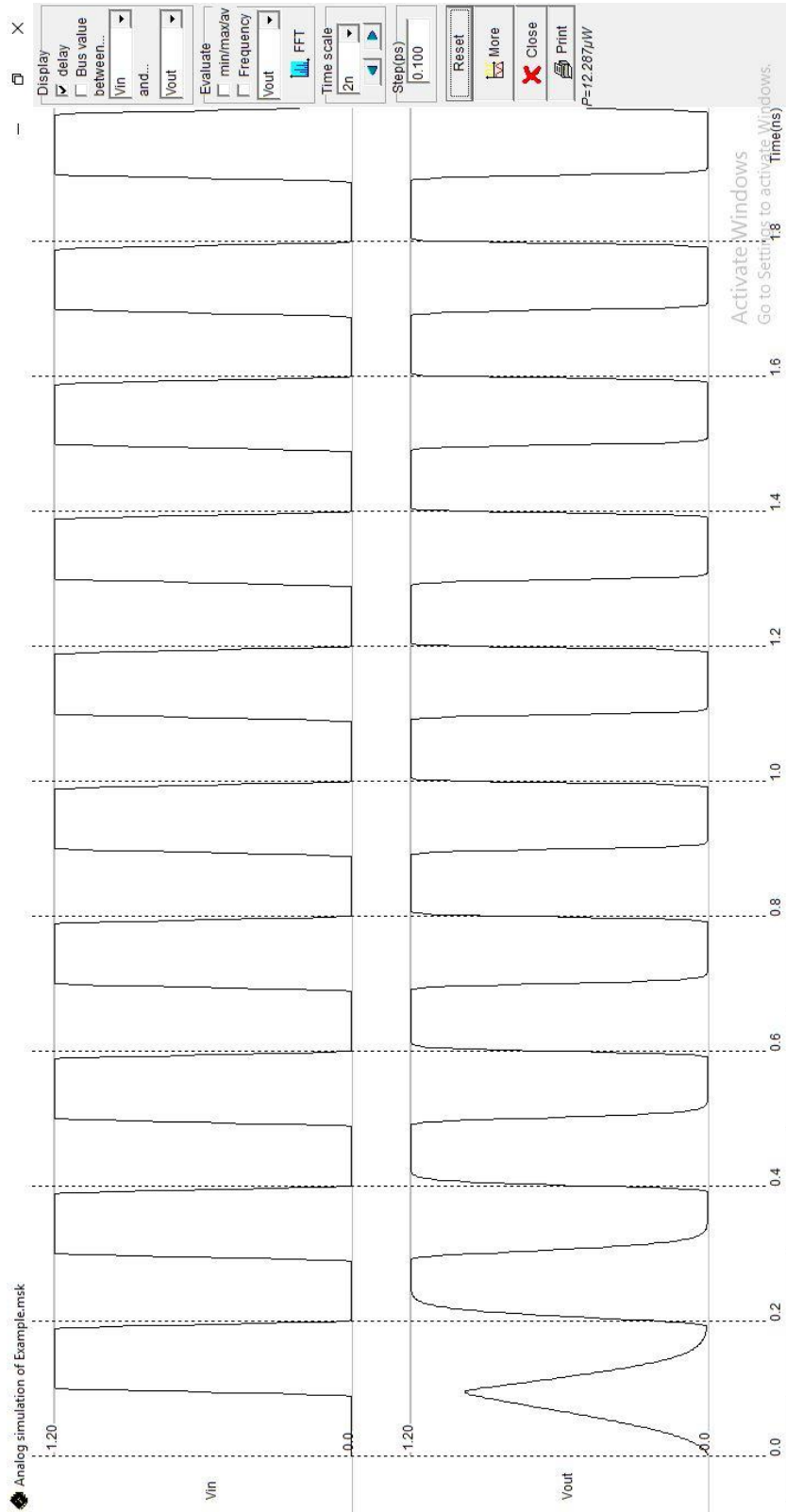


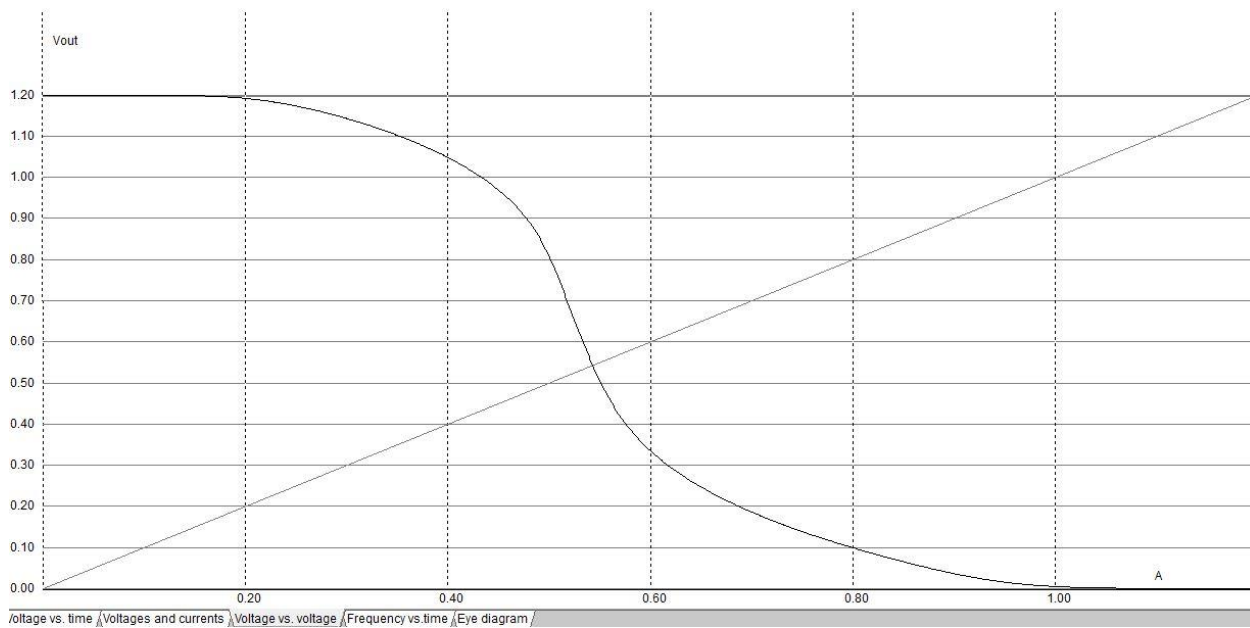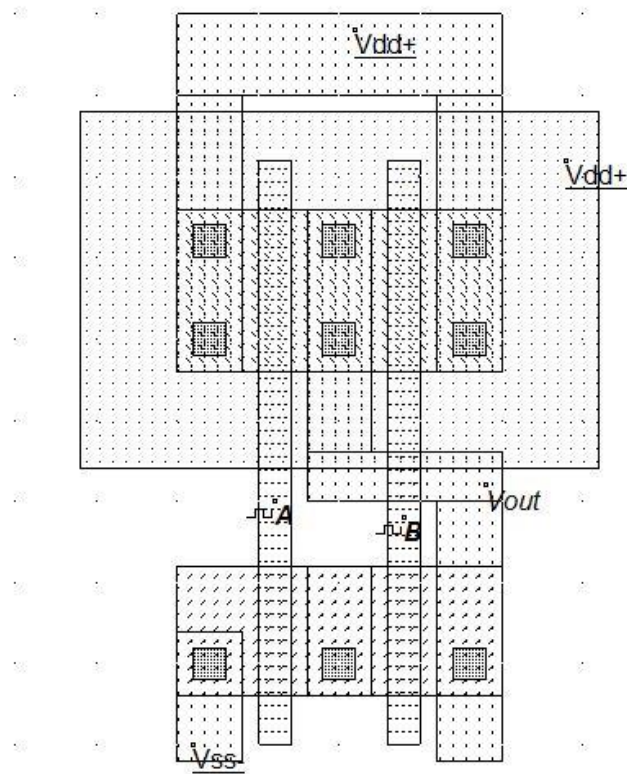
NAND GATE WITH SIZING

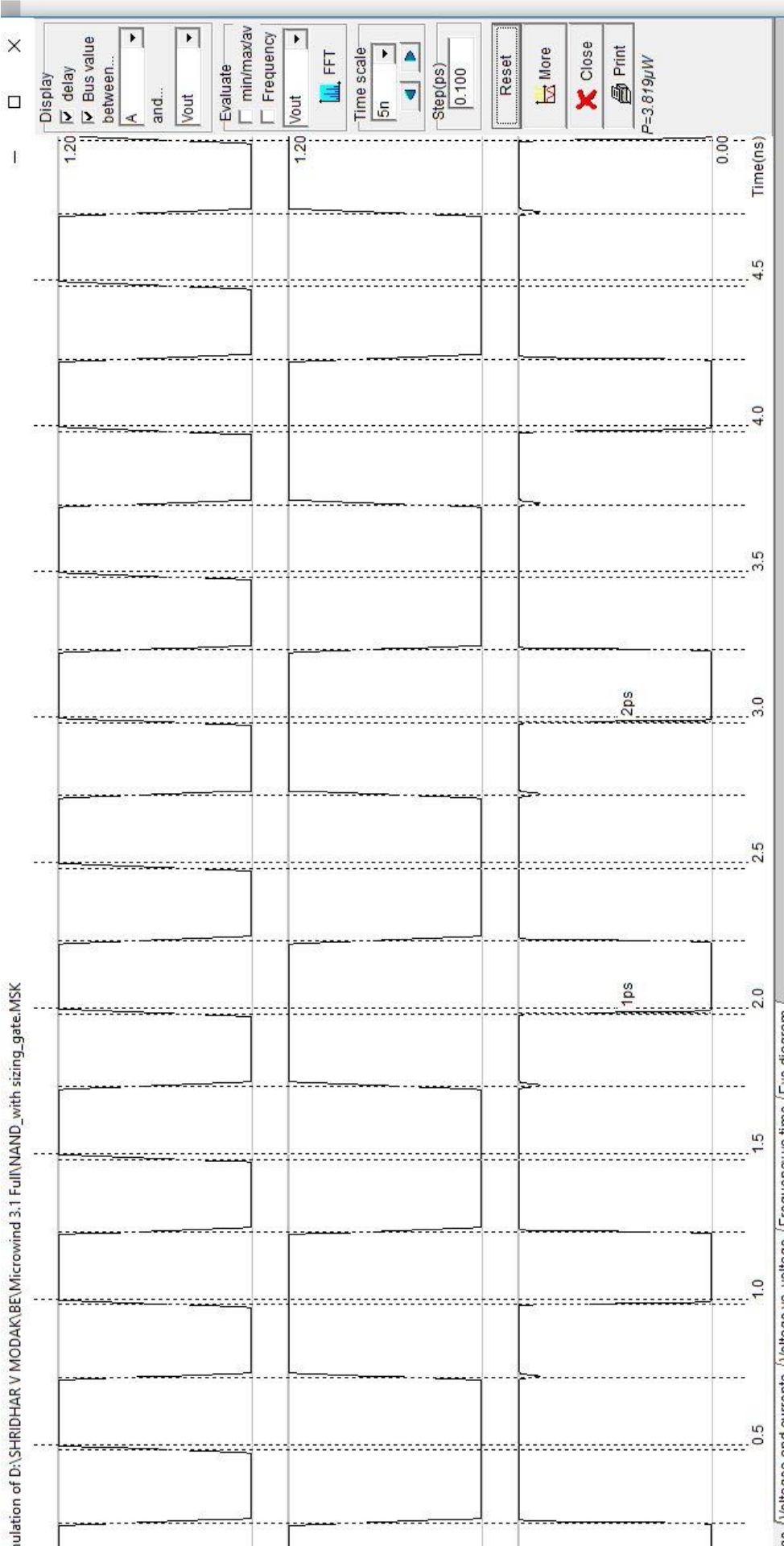

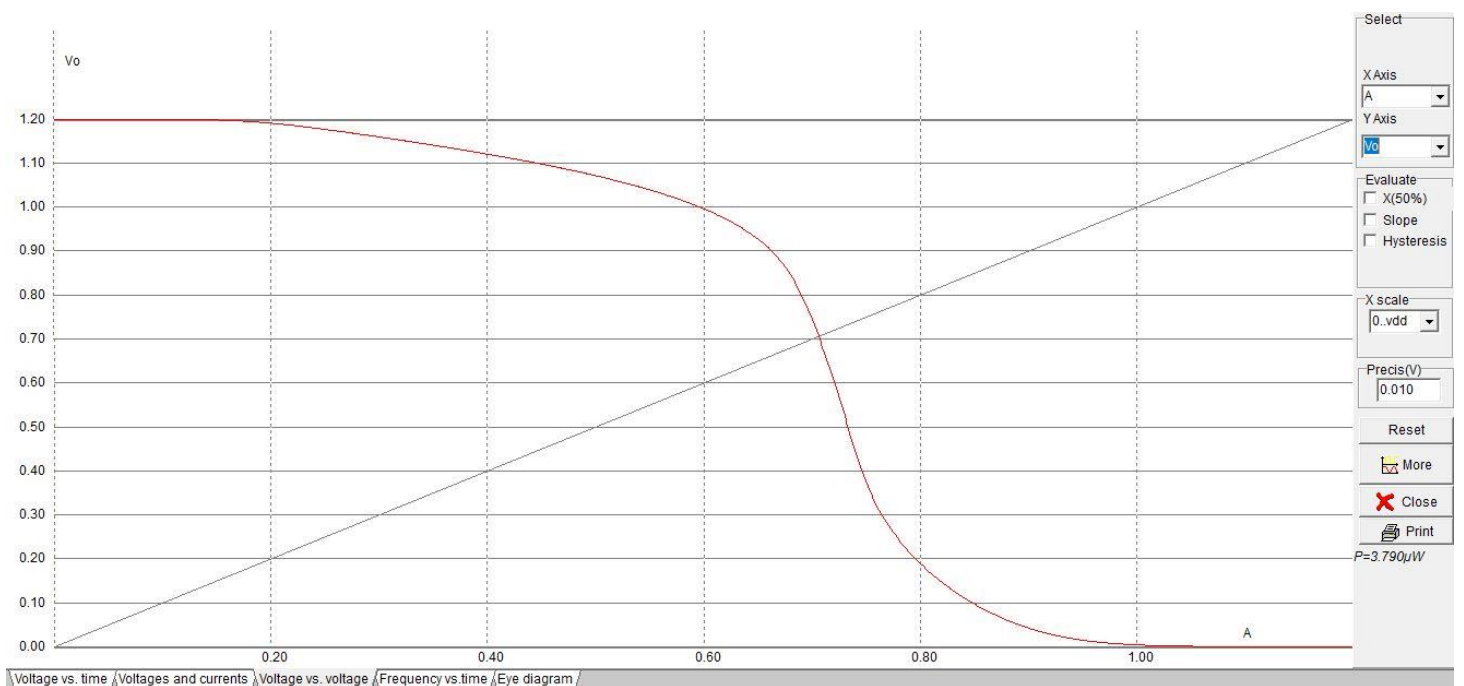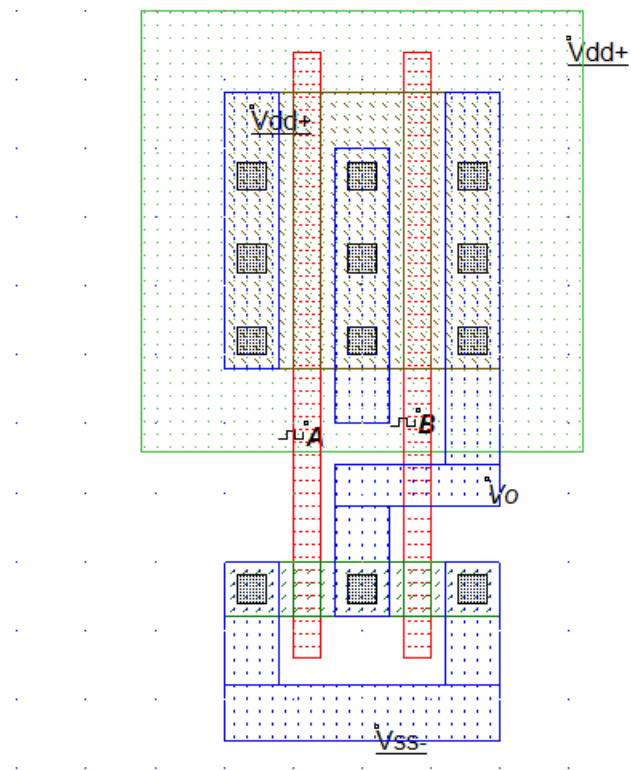NOR GATE WITH SIZING

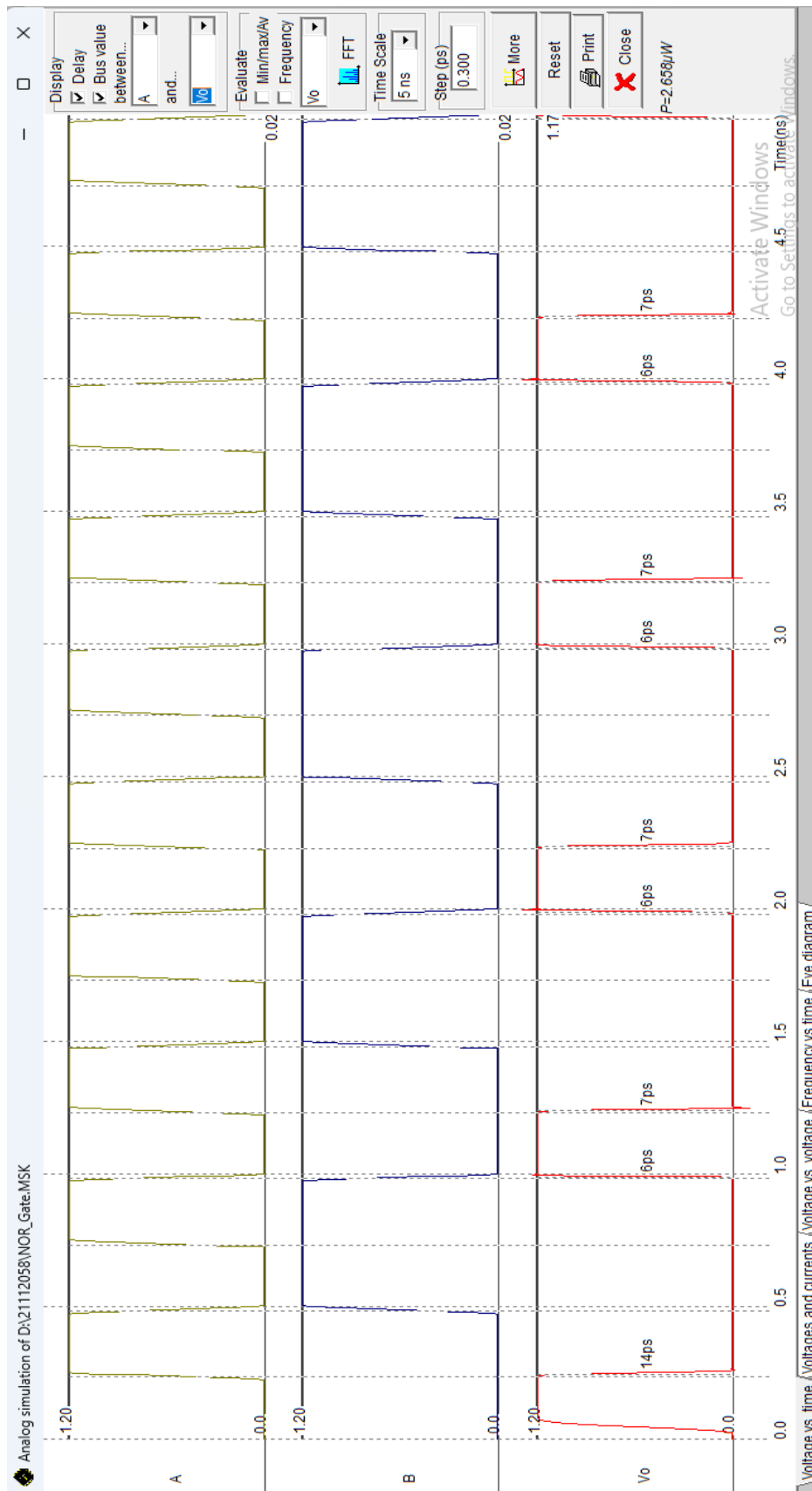

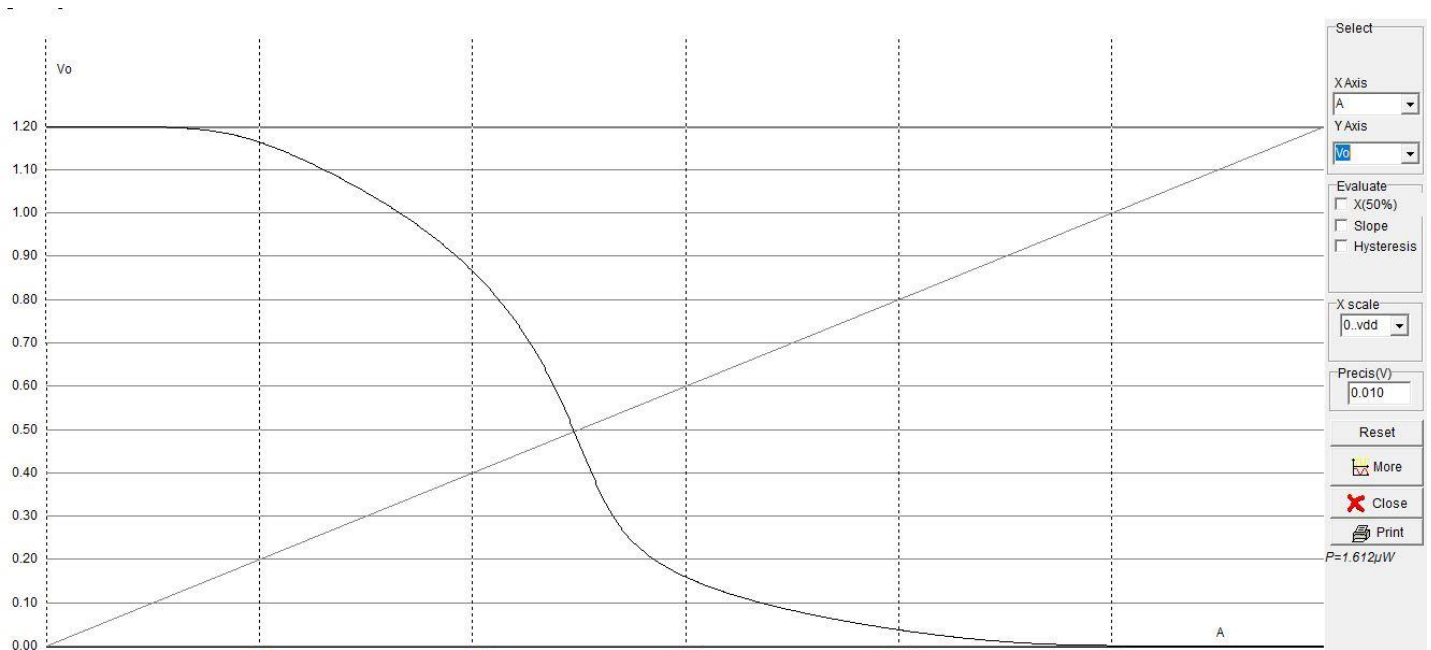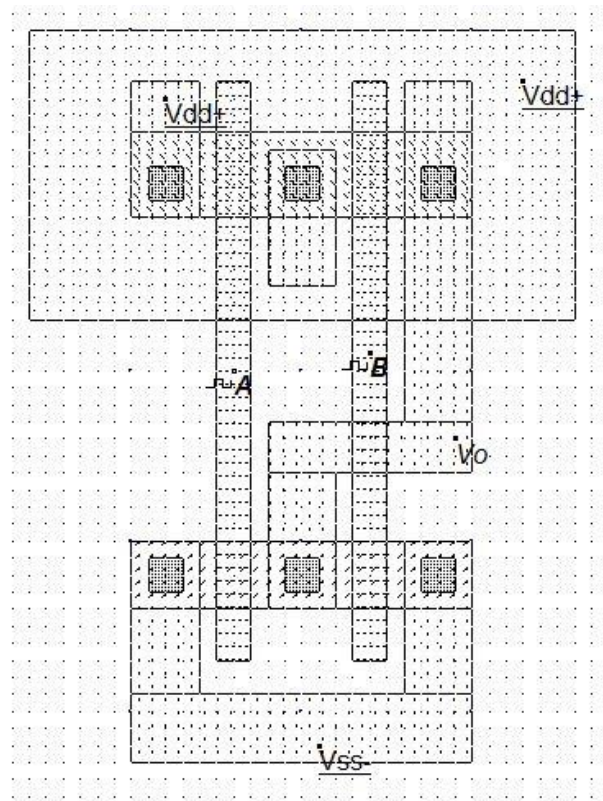NOR GATE WITHOUT SIZING

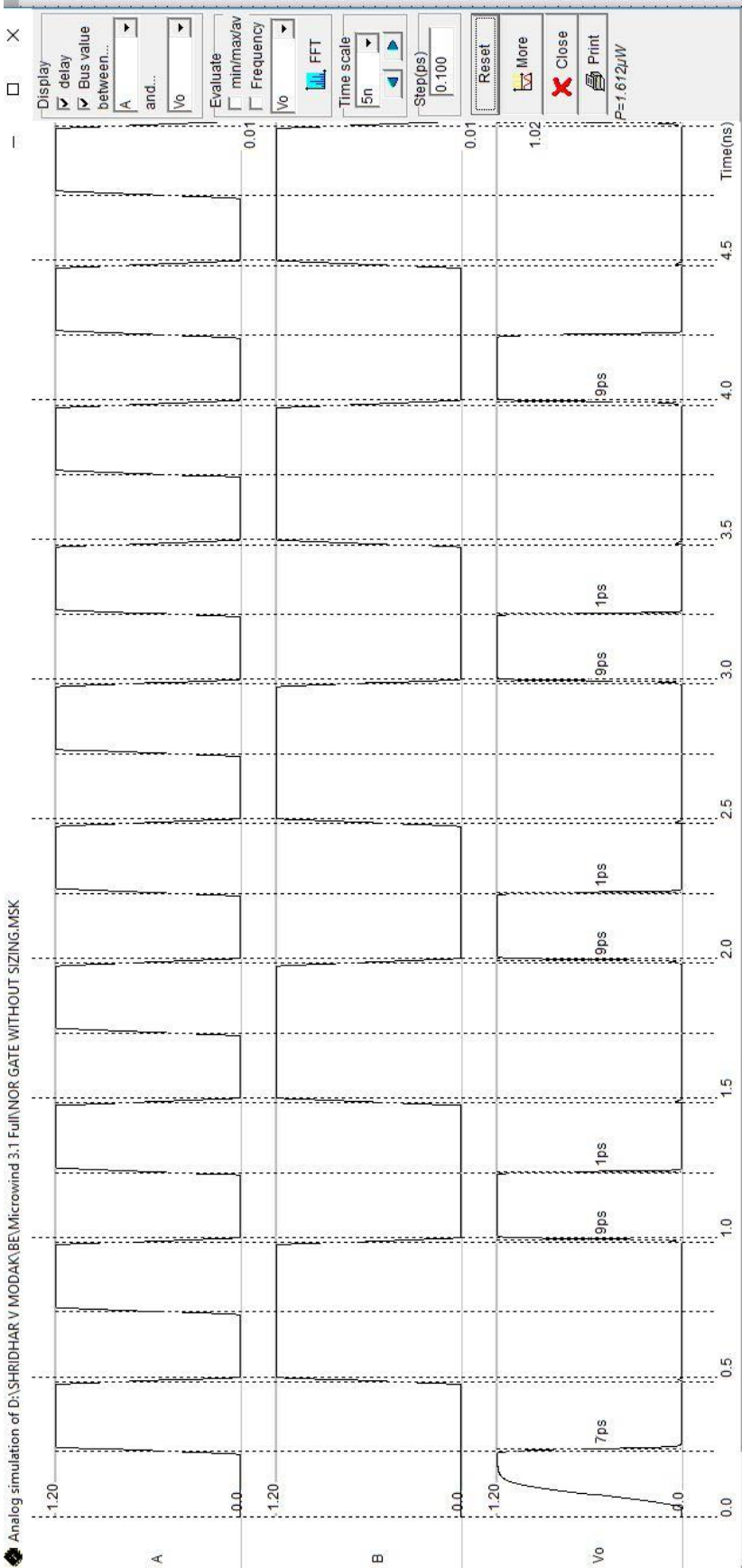

NAND GATE WITHOUT SIZING

